

Rectifiers



&

**UNIVERSITY
CENTRE**


What is a Rectifier

- A rectifier converts from AC to DC current
- They rely on Diodes to function
- They are essential in modern electronics to convert mains electricity into usable DC for appliances




What is a Diode

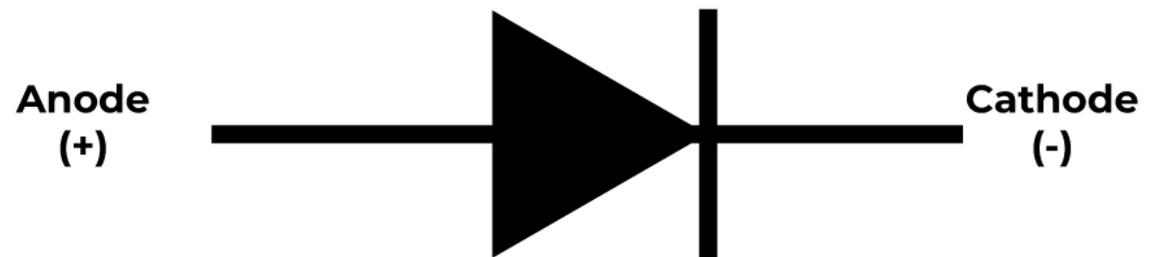- Diodes are electrical components that control the direction of flow of current
- This is because diodes are directional with a positive and negative side
- They let current flow one way but not the other




Half Wave Rectifiers

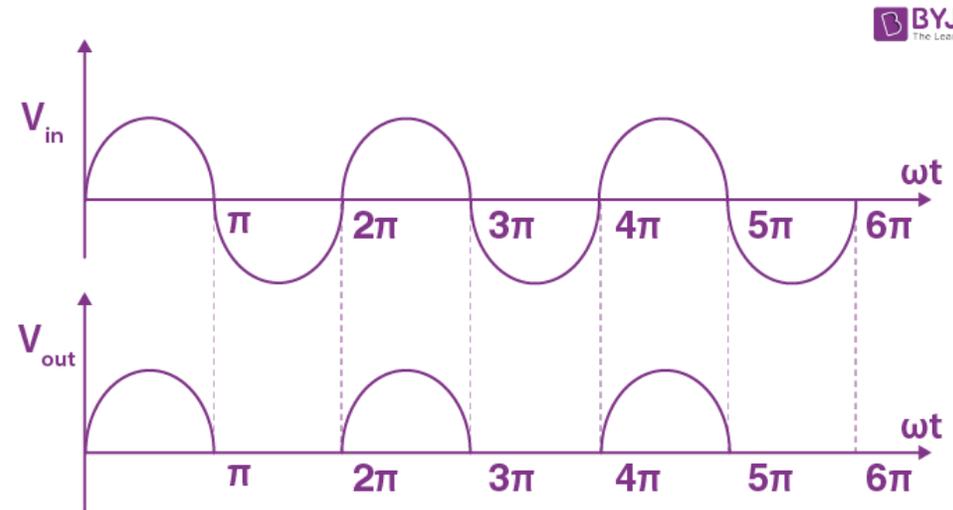- Half wave rectifiers only convert half the wave to DC
- This creates a pulsing DC output, this is sometimes referred to as “rippling”
- This is usually inadequate for modern scenarios as it is very inefficient converting under 50% of the original power
- This output requires heavy filtering to get a smooth DC output
- This is much cheaper and easier to build than full rectifiers though




Half Wave Rectifier Circuit

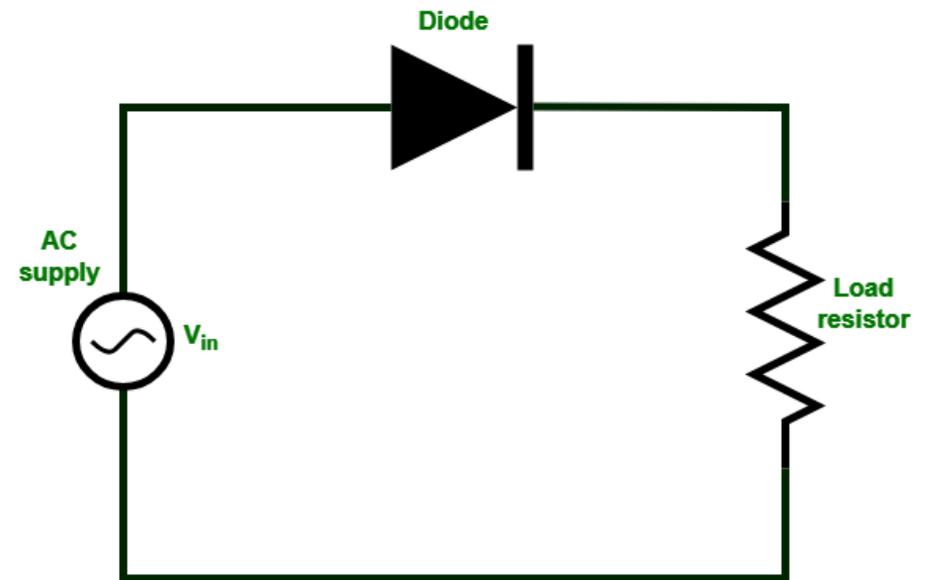- This is the circuit for a half wave rectifier
- The load resistor can be replaced by any load





Full Wave Rectifier

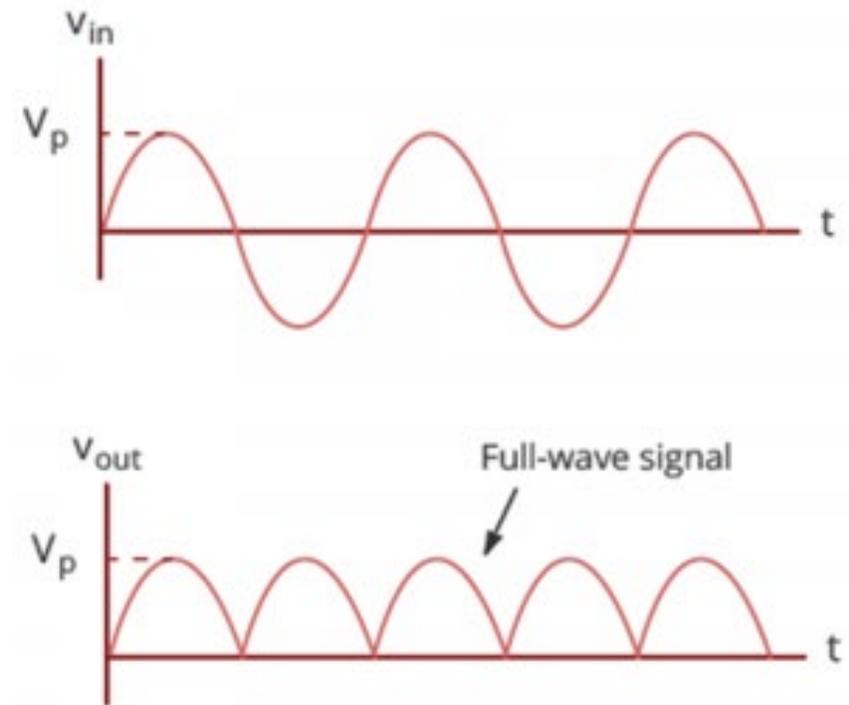- Full wave rectifiers convert the full AC wave to DC
- Still a pulsing DC but pulsing a lot faster, this is sometimes referred to as “rippling”
- Much more efficient than halfwave
- Uses two or four rectifiers to allow both halves of the AC waveform to pass
- Provides a higher average DC output
- A lot easier to filter to get a smooth DC output




Full Wave Rectifier (Centre-Tap)

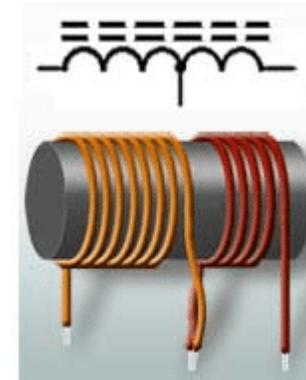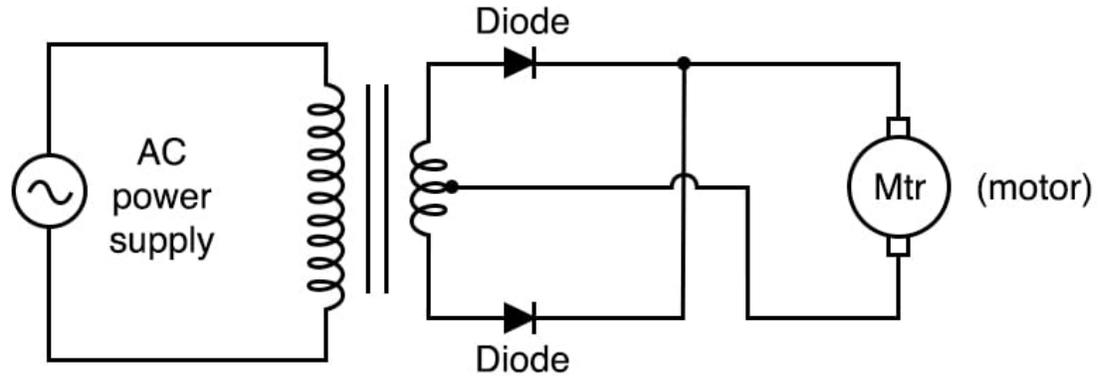- Uses a centre-tapped transformer and two diodes
- Each diode conducts alternating parts of the wave




Full Wave Rectifier (Bridge)

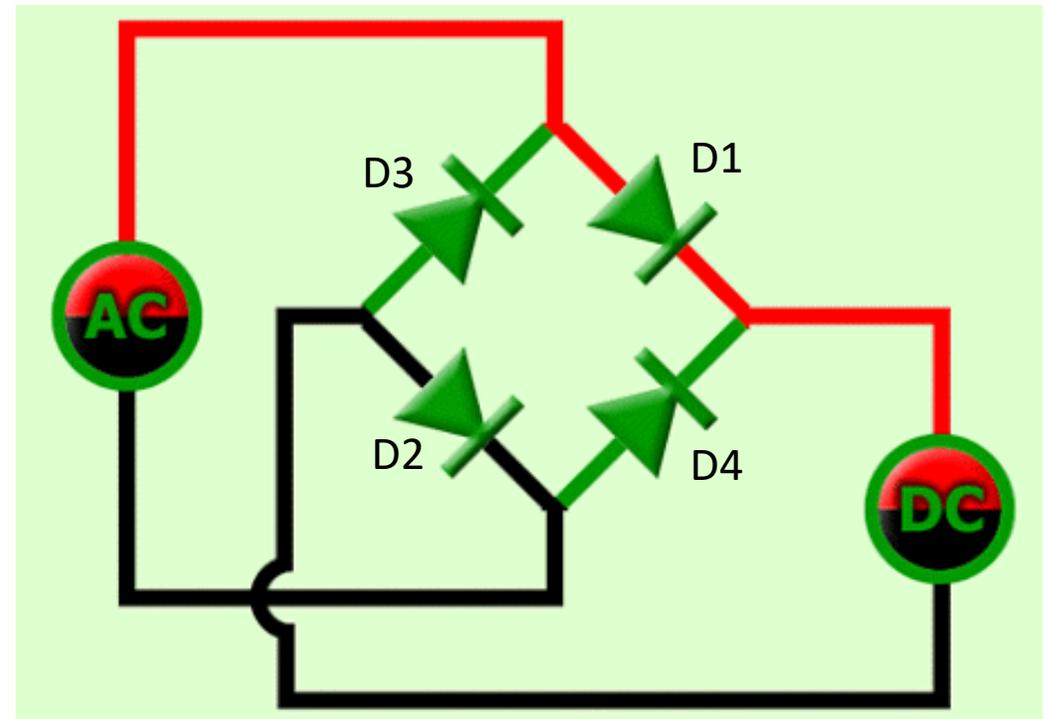- Uses a bridge constructed out of two pairs of diodes which work in unison
- The pairs are opposites (D1+D2) and (D3+D4)
- This is much cheaper and easier to construct as you don't need a centre-tapped inductor
- Provides higher efficiency and better voltage regulation



Filtering of Rectifier Outputs

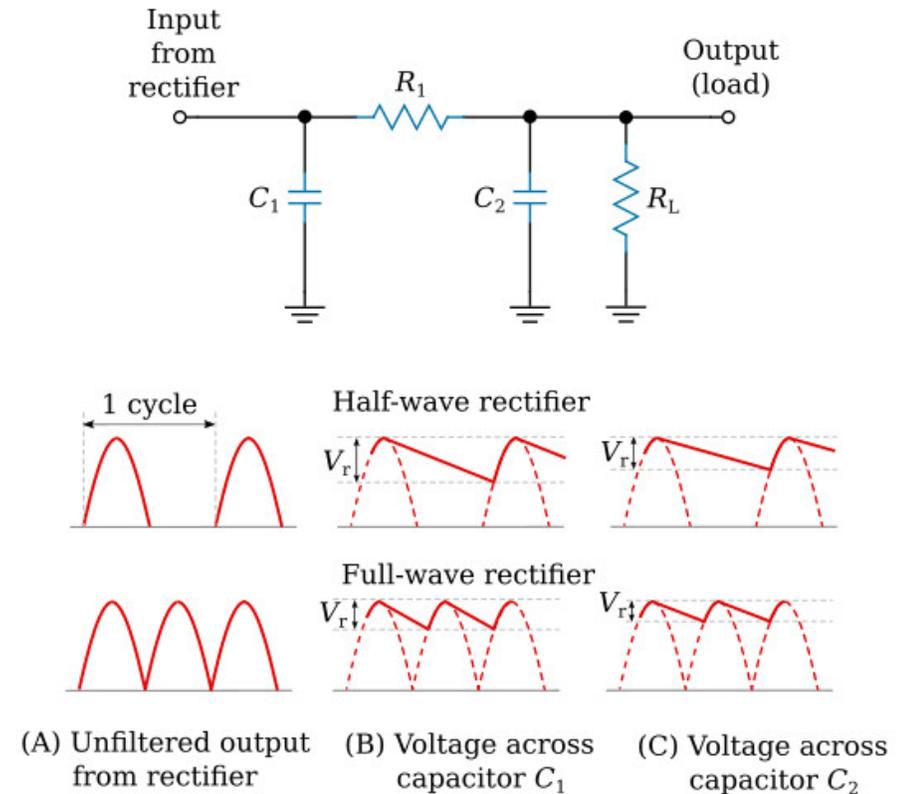- The output of a rectifier is filtered and “smoothed” using capacitors
- The capacitors take the spikes and then release them over time
- You will always be left with some rippling or pulsing however it will be a lot smoother



Equations

- Half Wave:

- $V_{DC} = \frac{V_m}{\pi}$

- $V_{rms} = \frac{V_m}{2}$

- $\gamma = \sqrt{\left(\frac{V_{rms}}{V_{DC}}\right)^2 - 1}$ <- Ripple Factor

- Full Wave:

- $V_{DC} = \frac{2V_m}{\pi}$

- $V_{rms} = \frac{V_m}{\sqrt{2}}$

- $\gamma = \sqrt{\left(\frac{V_{rms}}{V_{DC}}\right)^2 - 1}$ <- Ripple Factor